

AP Physics 1 Multiple Choice Questions - Chapter 12

1 If a current of 125 mA exists in a metal wire, how many electrons flow past a given cross section of the wire in 10 minutes?

- a 6.25×10^{21} electrons b 3.98×10^{19} electrons
c 5.35×10^{22} electrons d 4.66×10^{20} electrons

2 A wire carries a current of 1.6A. How many electrons per second pass a given point in the wire? Choose the best estimate.

- a 10^{17} b 10^{18}
c 10^{19} d 10^{20}
e 10^{21}

3 A proton beam in an accelerator carries a current of 125 microamps. If the beam is incident on a target, how many protons strike the target in a period of 23.0 seconds?

- a 1.8×10^{16} protons b 3.5×10^{19} protons
c 1.4×10^{15} protons d 8.5×10^{17} protons

AP Physics 1 Multiple Choice Questions - Chapter 12

1 An electric heater carries a current of 12 A when operating at a voltage of 120 V. what is the resistance of the electric heater?

- a 100 ohms b 10 ohms
c 1000 ohms d 0.1 ohms

2 Wire B has the same resistivity, twice the length, and twice the radius of wire A. If wire A has a resistance R , what is the resistance of wire B?

- a $4R$ b $2R$
c R d $R/2$
e $R/4$


3 Three wires are made of copper having circular cross sections. Wire 1 has a length L and a radius r . Wire 2 has a length L and a radius $2r$. Wire 3 has a length $2L$ and a radius $3r$.

Which wire has the smallest resistance?

- a Wire 1 b Wire 2
c Wire 3 d All three wires have the same resistance
e Not enough information given to answer the question

AP Physics 1 Multiple Choice Questions - Chapter 12

1

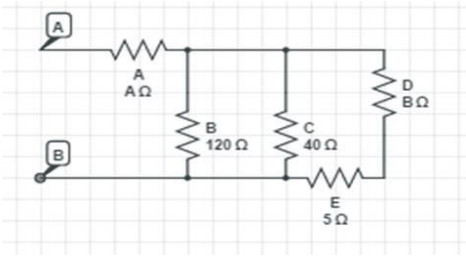

Using the circuit shown above, and assuming that $A = 10$ ohms and $B = 20$ ohms, calculate the equivalent resistance

- a 195 ohms
- b 23.64 ohms
- c 4.65 ohms
- d 13.08 ohms


- 2 Three resistors, A, B, and C, are connected in parallel and attached to a battery, with the resistance of A being the smallest and the resistance of C being the greatest. Which resistor carries the highest current?

- a A
- b B
- c C
- d All wires carry the same current
- e More information is needed to answer the question

- 3 Three resistors, A, B, and C, are connected in series in a closed loop with a battery, with the resistance of A being the smallest and the resistance of C the greatest. Across which resistor is the voltage drop the greatest?

- a A
- b B
- c C
- d The voltage drops are the same for each
- e More information is needed to answer the question

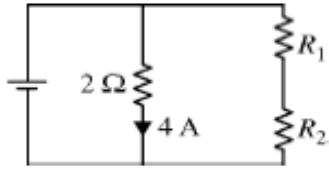
AP Physics 1 Multiple Choice Questions - Chapter 12



12.4

1 In the circuit shown above, the sum of the resistances of resistors R_1 and R_2 is 8Ω .
 What is the current through the battery?


- a 4 A
- b 5 A
- c 8 A
- d 20 A

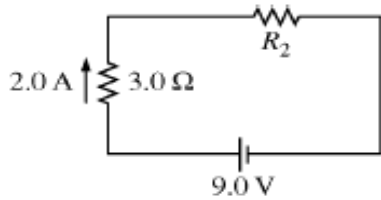

12.4

2 A 9.0 V battery and two resistors are connected in the circuit shown above. The current through the 3.0Ω resistor is 2.0 A . What is the potential difference across resistor R_2 ?

- a 9.0 V
- b 6.0 V
- c 3.0 V
- d 1.5 V

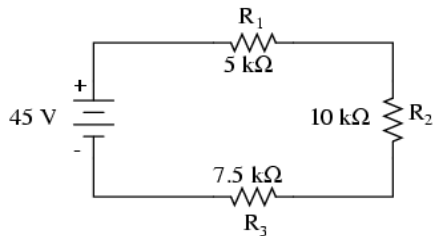


12.4

3 A 45 V battery and three resistors are connected in the circuit shown above. What is the current passing through the circuit?

- a 2 A
- b 0.005 A
- c 0.002 A
- d 5 A

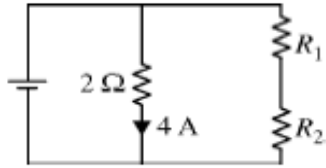AP Physics 1 Multiple Choice Questions - Chapter 12



12.5

- 1 In the circuit shown above, the sum of the resistances of resistors R_1 and R_2 is $8\ \Omega$. Resistor R_1 and the $2\ \Omega$ resistor are now swapped. How does the current in the right branch of the circuit change, and why?
- a The current does not change, because the total resistance does not change
 - b The current increases, because the total resistance will always decrease
 - c The current decreases, because the total resistance will always increase
 - d The change in current cannot be determined without knowing the resistances of R_1 and R_2 .





AP Physics 1 Multiple Choice Questions - Chapter 12

Circuit Element	Potential Difference (V)	Current (A)
Battery	10	8
Resistor R_1	6	8
Resistor R_2	4	3
Resistor R_3	4	5




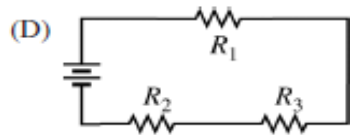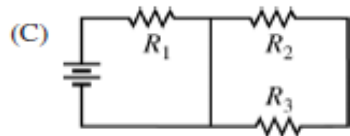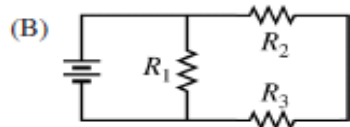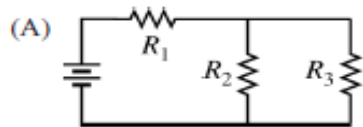12.5

- 2 The above table shows the potential difference and current for each circuit element in a circuit consisting of a battery and three resistors. Which of the following diagrams could represent the circuit?



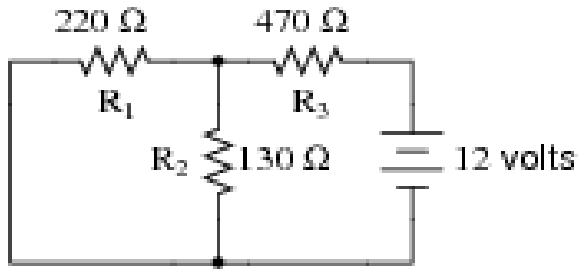AP Physics 1 Multiple Choice Questions - Chapter 12



12.5

- 3 A DC circuit is set up as shown above. What is the power dissipated in the third resistor R_3 ?
- a 222 mW
 - b 24 mW
 - c 85 mW
 - d 14 mW